

The Art Of Electronics - 2nd Edition

**Paul Horowitz** HARVARD UNIVERSITY

**Winfield Hill** ROWLAND INSTITUTE FOR SCIENCE, CAMBRIDGE, MASSACHUSETTS



## Contents

List of tables	xvi
Preface	xix
Preface to first edition	xxi
<b>CHAPTER 1</b>	
<b>FOUNDATIONS</b>	<b>1</b>
Introduction	1
Voltage, current, and resistance	2
1.01 Voltage and current	2
1.02 Relationship between voltage and current: resistors	4
1.03 Voltage dividers	8
1.04 Voltage and current sources	9
1.05 Thévenin's equivalent circuit	11
1.06 Small-signal resistance	13
Signals	15
1.07 Sinusoidal signals	15
1.08 Signal amplitudes and decibels	16
1.09 Other signals	17
1.10 Logic levels	19
1.11 Signal sources	19
Capacitors and ac circuits	20
1.12 Capacitors	20
1.13 $RC$ circuits: $V$ and $I$ versus time	23
1.14 Differentiators	25
1.15 Integrators	26
Inductors and transformers	28
1.16 Inductors	28
1.17 Transformers	28
Impedance and reactance	29
1.18 Frequency analysis of reactive circuits	30
1.19 $RC$ filters	35
1.20 Phasor diagrams	39
1.21 "Poles" and decibels per octave	40
1.22 Resonant circuits and active filters	41
1.23 Other capacitor applications	42
1.24 Thévenin's theorem generalized	44
Diodes and diode circuits	44
1.25 Diodes	44
1.26 Rectification	44
1.27 Power-supply filtering	45
1.28 Rectifier configurations for power supplies	46
1.29 Regulators	48
1.30 Circuit applications of diodes	48
1.31 Inductive loads and diode protection	52
Other passive components	53
1.32 Electromechanical devices	53
1.33 Indicators	57
1.34 Variable components	57
<i>Additional exercises</i>	58
<b>CHAPTER 2</b>	
<b>TRANSISTORS</b>	<b>61</b>
Introduction	61
2.01 First transistor model: current amplifier	62
Some basic transistor circuits	63
2.02 Transistor switch	63
2.03 Emitter follower	65

---

2.04 Emitter followers as voltage regulators	68
2.05 Emitter follower biasing	69
2.06 Transistor current source	72
2.07 Common-emitter amplifier	76
2.08 Unity-gain phase splitter	77
2.09 Transconductance	78
Ebers-Moll model applied to basic transistor circuits	79
2.10 Improved transistor model: transconductance amplifier	79
2.11 The emitter follower revisited	81
2.12 The common-emitter amplifier revisited	82
2.13 Biasing the common-emitter amplifier	84
2.14 Current mirrors	88
Some amplifier building blocks	91
2.15 Push-pull output stages	91
2.16 Darlington connection	94
2.17 Bootstrapping	96
2.18 Differential amplifiers	98
2.19 Capacitance and Miller effect	102
2.20 Field-effect transistors	104
Some typical transistor circuits	104
2.21 Regulated power supply	104
2.22 Temperature controller	105
2.23 Simple logic with transistors and diodes	107
Self-explanatory circuits	107
2.24 Good circuits	107
2.25 Bad circuits	107
<i>Additional exercises</i>	107
<b>CHAPTER 3</b>	
<b>FIELD-EFFECT TRANSISTORS</b>	<b>113</b>
Introduction	113
3.01 FET characteristics	114
3.02 FET types	117
3.03 Universal FET characteristics	119
3.04 FET drain characteristics	121
3.05 Manufacturing spread of FET characteristics	122
<b>Basic FET circuits</b>	<b>124</b>
3.06 JFET current sources	125
3.07 FET amplifiers	129
3.08 Source followers	133
3.09 FET gate current	135
3.10 FETs as variable resistors	138
FET switches	140
3.11 FET analog switches	141
3.12 Limitations of FET switches	144
3.13 Some FET analog switch examples	151
3.14 MOSFET logic and power switches	153
3.15 MOSFET handling precautions	169
Self-explanatory circuits	171
3.16 Circuit ideas	171
3.17 Bad circuits	171 vskip6pt
<b>CHAPTER 4</b>	
<b>FEEDBACK AND OPERATIONAL AMPLIFIERS</b>	<b>175</b>
Introduction	175
4.01 Introduction to feedback	175
4.02 Operational amplifiers	176
4.03 The golden rules	177
Basic op-amp circuits	177
4.04 Inverting amplifier	177
4.05 Noninverting amplifier	178
4.06 Follower	179
4.07 Current sources	180
4.08 Basic cautions for op-amp circuits	182
An op-amp smorgasbord	183
4.09 Linear circuits	183
4.10 Nonlinear circuits	187
A detailed look at op-amp behavior	188
4.11 Departure from ideal op-amp performance	189
4.12 Effects of op-amp limitations on circuit behavior	193
4.13 Low-power and programmable op-amps	210

---

A detailed look at selected op-amp circuits	213	4.37 Bad circuits	250
4.14 Logarithmic amplifier	213	<i>Additional exercises</i>	251
4.15 Active peak detector	217	<b>CHAPTER 5</b>	
4.16 Sample-and-hold	220	<b>ACTIVE FILTERS AND</b>	
4.17 Active clamp	221	<b>OSCILLATORS</b>	263
4.18 Absolute-value circuit	221	Active filters	263
4.19 Integrators	222	5.01 Frequency response with <i>RC</i>	
4.20 Differentiators	224	filters	263
Op-amp operation with a single power supply	224	5.02 Ideal performance with <i>LC</i>	
4.21 Biasing single-supply ac amplifiers	225	filters	265
4.22 Single-supply op-amps	225	5.03 Enter active filters: an overview	266
Comparators and Schmitt trigger	229	5.04 Key filter performance criteria	267
4.23 Comparators	229	5.05 Filter types	268
4.24 Schmitt trigger	231	Active filter circuits	272
Feedback with finite-gain amplifiers	232	5.06 VCVS circuits	273
4.25 Gain equation	232	5.07 VCVS filter design using our simplified table	274
4.26 Effects of feedback on amplifier circuits	233	5.08 State-variable filters	276
4.27 Two examples of transistor amplifiers with feedback	236	5.09 Twin-T notch filters	279
Some typical op-amp circuits	238	5.10 Gyrator filter realizations	281
4.28 General-purpose lab amplifier	238	5.11 Switched-capacitor filters	281
4.29 Voltage-controlled oscillator	240	<b>Oscillators</b>	284
4.30 JFET linear switch with $R_{ON}$ compensation	241	5.12 Introduction to oscillators	284
4.31 TTL zero-crossing detector	242	5.13 Relaxation oscillators	284
4.32 Load-current-sensing circuit	242	5.14 The classic timer chip: the 555	286
Feedback amplifier frequency compensation	242	5.15 Voltage-controlled oscillators	291
4.33 Gain and phase shift versus frequency	243	5.16 Quadrature oscillators	291
4.34 Amplifier compensation methods	245	5.17 Wien bridge and <i>LC</i> oscillators	296
4.35 Frequency response of the feedback network	247	5.18 <i>LC</i> oscillators	297
Self-explanatory circuits	250	5.19 Quartz-crystal oscillators	300
4.36 Circuit ideas	250	Self-explanatory circuits	303
		5.20 Circuit ideas	303
		<i>Additional exercises</i>	303
		<b>CHAPTER 6</b>	
		<b>VOLTAGE REGULATORS AND POWER</b>	
		<b>CIRCUITS</b>	307
		Basic regulator circuits with the classic 723	307

- 
- 6.01 The 723 regulator 307
  - 6.02 Positive regulator 309
  - 6.03 High-current regulator 311
  - Heat and power design 312
  - 6.04 Power transistors and heat sinking 312
  - 6.05 Foldback current limiting 316
  - 6.06 Overvoltage crowbars 317
  - 6.07 Further considerations in high-current power-supply design 320
  - 6.08 Programmable supplies 321
  - 6.09 Power-supply circuit example 323
  - 6.10 Other regulator ICs 325
  - The unregulated supply 325
  - 6.11 ac line components 326
  - 6.12 Transformer 328
  - 6.13 dc components 329
  - Voltage references 331
  - 6.14 Zener diodes 332
  - 6.15 Bandgap ( $V_{BE}$ ) reference 335
  - Three-terminal and four-terminal regulators 341
  - 6.16 Three-terminal regulators 341
  - 6.17 Three-terminal adjustable regulators 344
  - 6.18 Additional comments about 3-terminal regulators 345
  - 6.19 Switching regulators and dc-dc converters 355
  - Special-purpose power-supply circuits 368
  - 6.20 High-voltage regulators 368
  - 6.21 Low-noise, low-drift supplies 374
  - 6.22 Micropower regulators 376
  - 6.23 Flying-capacitor (charge pump) voltage converters 377
  - 6.24 Constant-current supplies 379
  - 6.25 Commercial power-supply modules 382
  - Self-explanatory circuits 384
  - 6.26 Circuit ideas 384
  - 6.27 Bad circuits 384
  - Additional exercises* 384
- CHAPTER 7
  - PRECISION CIRCUITS AND LOW-NOISE TECHNIQUES 391
  - Precision op-amp design techniques 391
  - 7.01 Precision versus dynamic range 391
  - 7.02 Error budget 392
  - 7.03 Example circuit: precision amplifier with automatic null offset 392
  - 7.04 A precision-design error budget 394
  - 7.05 Component errors 395
  - 7.06 Amplifier input errors 396
  - 7.07 Amplifier output errors 403
  - 7.08 Auto-zeroing (chopper-stabilized) amplifiers 415
  - Differential and instrumentation amplifiers 421
  - 7.09 Differencing amplifier 421
  - 7.10 Standard three-op-amp instrumentation amplifier 425
  - Amplifier noise 428
  - 7.11 Origins and kinds of noise 430
  - 7.12 Signal-to-noise ratio and noise figure 433
  - 7.13 Transistor amplifier voltage and current noise 436
  - 7.14 Low-noise design with transistors 438
  - 7.15 FET noise 443
  - 7.16 Selecting low-noise transistors 445
  - 7.17 Noise in differential and feedback amplifiers 445
  - Noise measurements and noise sources 449
  - 7.18 Measurement without a noise source 449
  - 7.19 Measurement with noise source 450
  - 7.20 Noise and signal sources 452
  - 7.21 Bandwidth limiting and rms voltage measurement 453
  - 7.22 Noise potpourri 454

- Interference: shielding and grounding 455
- 7.23 Interference 455
- 7.24 Signal grounds 457
- 7.25 Grounding between instruments 457
- Self-explanatory circuits 466
- 7.26 Circuit ideas 466
- Additional exercises* 466
- CHAPTER 8**  
**DIGITAL ELECTRONICS 471**
- Basic logic concepts 471
- 8.01 Digital versus analog 471
- 8.02 Logic states 472
- 8.03 Number codes 473
- 8.04 Gates and truth tables 478
- 8.05 Discrete circuits for gates 480
- 8.06 Gate circuit example 481
- 8.07 Assertion-level logic notation 482
- TTL and CMOS 484
- 8.08 Catalog of common gates 484
- 8.09 IC gate circuits 485
- 8.10 TTL and CMOS characteristics 486
- 8.11 Three-state and open-collector devices 487
- Combinational logic 490
- 8.12 Logic identities 491
- 8.13 Minimization and Karnaugh maps 492
- 8.14 Combinational functions available as ICs 493
- 8.15 Implementing arbitrary truth tables 500
- Sequential logic 504
- 8.16 Devices with memory: flip-flops 504
- 8.17 Clocked flip-flops 507
- 8.18 Combining memory and gates: sequential logic 512
- 8.19 Synchronizer 515
- Monostable multivibrators 517
- 8.20 One-shot characteristics 517
- 8.21 Monostable circuit example 519
- 8.22 Cautionary notes about monostables 519
- 8.23 Timing with counters 522
- Sequential functions available as ICs 523
- 8.24 Latches and registers 523
- 8.25 Counters 524
- 8.26 Shift registers 525
- 8.27 Sequential PALs 527
- 8.28 Miscellaneous sequential functions 541
- Some typical digital circuits 544
- 8.29 Modulo- $n$  counter: a timing example 544
- 8.30 Multiplexed LED digital display 546
- 8.31 Sidereal telescope drive 548
- 8.32 An  $n$ -pulse generator 548
- Logic pathology 551
- 8.33 dc problems 551
- 8.34 Switching problems 552
- 8.35 Congenital weaknesses of TTL and CMOS 554
- Self-explanatory circuits 556
- 8.36 Circuit ideas 556
- 8.37 Bad circuits 556
- Additional exercises* 556
- CHAPTER 9**  
**DIGITAL MEETS ANALOG 565**
- CMOS and TTL logic interfacing 565
- 9.01 Logic family chronology 565
- 9.02 Input and output characteristics 570
- 9.03 Interfacing between logic families 572
- 9.04 Driving CMOS and TTL inputs 575
- 9.05 Driving digital logic from comparators and op-amps 577

- 9.06 Some comments about logic inputs 579
- 9.07 Comparators 580
- 9.08 Driving external digital loads from CMOS and TTL 582
- 9.09 NMOS LSI interfacing 588
- 9.10 Opto-electronics 590
- Digital signals and long wires 599
- 9.11 On-board interconnections 599
- 9.12 Intercard connections 601
- 9.13 Data buses 602
- 9.14 Driving cables 603
- Analog/digital conversion 612
- 9.15 Introduction to A/D conversion 612
- 9.16 Digital-to-analog converters (DACs) 614
- 9.17 Time-domain (averaging) DACs 618
- 9.18 Multiplying DACs 619
- 9.19 Choosing a DAC 619
- 9.20 Analog-to-digital converters 621
- 9.21 Charge-balancing techniques 626
- 9.22 Some unusual A/D and D/A converters 630
- 9.23 Choosing an ADC 631
- Some A/D conversion examples 636
- 9.24 16-Channel A/D data-acquisition system 636
- 9.25  $3\frac{1}{2}$ -Digit voltmeter 638
- 9.26 Coulomb meter 640
- Phase-locked loops 641
- 9.27 Introduction to phase-locked loops 641
- 9.28 PLL design 646
- 9.29 Design example: frequency multiplier 647
- 9.30 PLL capture and lock 651
- 9.31 Some PLL applications 652
- Pseudo-random bit sequences and noise generation 655
- 9.32 Digital noise generation 655
- 9.33 Feedback shift register sequences 655
- 9.34 Analog noise generation from maximal-length sequences 658
- 9.35 Power spectrum of shift register sequences 658
- 9.36 Low-pass filtering 660
- 9.37 Wrap-up 661
- 9.38 Digital filters 664
- Self-explanatory circuits 667
- 9.39 Circuit ideas 667
- 9.40 Bad circuits 668
- Additional exercises* 668
- CHAPTER 10  
MICROCOMPUTERS 673
- Minicomputers, microcomputers, and microprocessors 673
- 10.01 Computer architecture 674
- A computer instruction set 678
- 10.02 Assembly language and machine language 678
- 10.03 Simplified 8086/8 instruction set 679
- 10.04 A programming example 683
- Bus signals and interfacing 684
- 10.05 Fundamental bus signals: data, address, strobe 684
- 10.06 Programmed I/O: data out 685
- 10.07 Programmed I/O: data in 689
- 10.08 Programmed I/O: status registers 690
- 10.09 Interrupts 693
- 10.10 Interrupt handling 695
- 10.11 Interrupts in general 697
- 10.12 Direct memory access 701
- 10.13 Summary of the IBM PC's bus signals 704
- 10.14 Synchronous versus asynchronous bus communication 707
- 10.15 Other microcomputer buses 708
- 10.16 Connecting peripherals to the computer 711

---

Software system concepts	714	CHAPTER 12	
10.17 Programming	714	ELECTRONIC CONSTRUCTION	
10.18 Operating systems, files, and use of memory	716	TECHNIQUES	827
Data communications concepts	719	Prototyping methods	827
10.19 Serial communication and ASCII	720	12.01 Breadboards	827
10.20 Parallel communication: Centronics, SCSI, IPI, GPIB (488)	730	12.02 PC prototyping boards	828
10.21 Local area networks	734	12.03 Wire-Wrap panels	828
10.22 Interface example: hardware data packing	736	Printed circuits	830
10.23 Number formats	738	12.04 PC board fabrication	830
CHAPTER 11		12.05 PC board design	835
MICROPROCESSORS	743	12.06 Stuffing PC boards	838
A detailed look at the 68008	744	12.07 Some further thoughts on PC boards	840
11.01 Registers, memory, and I/O	744	12.08 Advanced techniques	841
11.02 Instruction set and addressing	745	Instrument construction	852
11.03 Machine-language representation	750	12.09 Housing circuit boards in an instrument	852
11.04 Bus signals	753	12.10 Cabinets	854
A complete design example: analog signal averager	760	12.11 Construction hints	855
11.05 Circuit design	760	12.12 Cooling	855
11.06 Programming: defining the task	774	12.13 Some electrical hints	858
11.07 Programming: details	777	12.14 Where to get components	860
11.08 Performance	796	CHAPTER 13	
11.09 Some afterthoughts	797	HIGH-FREQUENCY AND HIGH-SPEED	
Microprocessor support chips	799	TECHNIQUES	863
11.10 Medium-scale integration	800	High-frequency amplifiers	863
11.11 Peripheral LSI chips	802	13.01 Transistor amplifiers at high frequencies: first look	863
11.12 Memory	812	13.02 High-frequency amplifiers: the ac model	864
11.13 Other microprocessors	820	13.03 A high-frequency calculation example	866
11.14 Emulators, development systems, logic analyzers, and evaluation boards	821	13.04 High-frequency amplifier configurations	868
		13.05 A wideband design example	869
		13.06 Some refinements to the ac model	872
		13.07 The shunt-series pair	872
		13.08 Modular amplifiers	873
		Radiofrequency circuit elements	879
		13.09 Transmission lines	879



13.10 Stubs, baluns, and transformers	881	Power sources	920
13.11 Tuned amplifiers	882	14.02 Battery types	920
13.12 Radiofrequency circuit elements	884	14.03 Wall-plug-in units	931
13.13 Measuring amplitude or power	888	14.04 Solar cells	932
Radiofrequency communications:		14.05 Signal currents	933
AM	892	Power switching and micropower regulators	938
13.14 Some communications concepts	892	14.06 Power switching	938
13.15 Amplitude modulation	894	14.07 Micropower regulators	941
13.16 Superheterodyne receiver	895	14.08 Ground reference	944
Advanced modulation methods	897	14.09 Micropower voltage references and temperature sensors	948
13.17 Single sideband	897	Linear micropower design techniques	948
13.18 Frequency modulation	898	14.10 Problems of micropower linear design	950
13.19 Frequency-shift keying	900	14.11 Discrete linear design example	950
13.20 Pulse-modulation schemes	900	14.12 Micropower operational amplifiers	951
Radiofrequency circuit tricks	902	14.13 Micropower comparators	965
13.21 Special construction techniques	902	14.14 Micropower timers and oscillators	965
13.22 Exotic RF amplifiers and devices	903	Micropower digital design	969
High-speed switching	904	14.15 CMOS families	969
13.23 Transistor model and equations	905	14.16 Keeping CMOS low power	970
13.24 Analog modeling tools	908	14.17 Micropower microprocessors and peripherals	974
Some switching-speed examples	909	14.18 Microprocessor design example: degree-day logger	978
13.25 High-voltage driver	909	Self-explanatory circuits	985
13.26 Open-collector bus driver	910	14.19 Circuit ideas	985
13.27 Example: photomultiplier preamp	911	CHAPTER 15	
Self-explanatory circuits	913	MEASUREMENTS AND SIGNAL PROCESSING	987
13.28 Circuit ideas	913	Overview	987
<i>Additional exercises</i>	913	Measurement transducers	988
CHAPTER 14		15.01 Temperature	988
LOW-POWER DESIGN	917	15.02 Light level	996
Introduction	917	15.03 Strain and displacement	1001
14.01 Low-power applications	918		

---

15.04 Acceleration, pressure, force, velocity 1004	APPENDICES 1043
15.05 Magnetic field 1007	Appendix A
15.06 Vacuum gauges 1007	The oscilloscope 1045
15.07 Particle detectors 1008	Appendix B
15.08 Biological and chemical voltage probes 1012	Math review 1050
Precision standards and precision measurements 1016	Appendix C
15.09 Frequency standards 1016	The 5% resistor color code 1053
15.10 Frequency, period, and time- interval measurements 1019	Appendix D
15.11 Voltage and resistance standards and measurements 1025	1% Precision resistors 1054
Bandwidth-narrowing techniques 1026	Appendix E
15.12 The problem of signal-to-noise ratio 1026	How to draw schematic diagrams 1056
15.13 Signal averaging and multichannel averaging 1026	Appendix F
15.14 Making a signal periodic 1030	Load lines 1059
15.15 Lock-in detection 1031	Appendix G
15.16 Pulse-height analysis 1034	Transistor saturation 1062
15.17 Time-to-amplitude converters 1035	Appendix H
Spectrum analysis and Fourier transforms 1035	LC Butterworth filters 1064
15.18 Spectrum analyzers 1035	Appendix I
15.19 Off-line spectrum analysis 1038	Electronics magazines and journals 1068
Self-explanatory circuits 1038	Appendix J
15.20 Circuit ideas 1038	IC prefixes 1069
	Appendix K
	Data sheets 1072
	2N4400-1 NPN transistor 1073
	LF411-12 JFET operational amplifier 1078
	LM317 3-terminal adjustable regulator 1086
	Bibliography 1095
	Index 1101